


How to design for 6V6 Single Ended Power Stage

6V6 シングル動作回路の 設計方法

Junichi Kubota


What is 6V6?

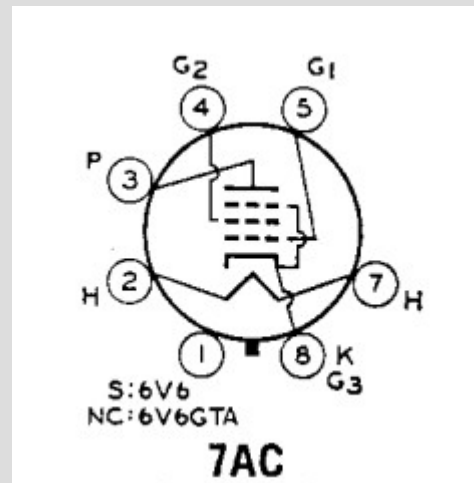- Middle size Beam Power Pentode
- Heater 6.3V/0.45A
- Maximum Rating
 - Plate 350V
 - G2 315V
 - Plate Dissipation 14 watts
 - G2 input 2.2watts



6V6ってどんな真空管?

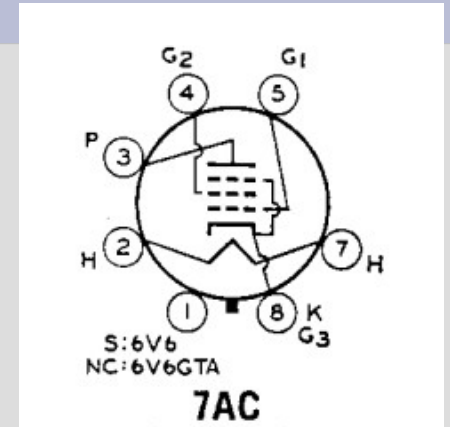- 中出力のビーム 5 極管
- ヒーター定格 6.3V/0.45A
- 最大定格
プレート 350V
スクリーングリッド 315V
プレート損失 14 watts
G2損失 2.2watts



Class A1 Amplifier


TYPICAL OPERATION

Plate Voltage	180	250	315	volts
Grid-No.2 Voltage	180	250	225	volts
Grid-No.1 (Control-Grid) Voltage	—8.5	—12.5	—13	volts
Peak AF Grid-No.1 Voltage	8.5	12.5	13	volts
Zero-Signal Plate Current	29	45	34	mA
Maximum-Signal Plate Current	30	47	35	mA
Zero-Signal Grid-No.2 Current	3	4.5	2.2	mA
Maximum-Signal Grid-No.2 Current	4	7	6	mA
Plate Resistance (Approx.)	50000	50000	80000	ohms
Transconductance	3700	4100	3750	μ mhos
Load Resistance	5500	5000	8500	ohms
Total Harmonic Distortion	8	8	12	per cent
Maximum-Signal Power Output	2	4.5	5.5	watts


Design for self bias

TYPICAL OPERATION

Plate Voltage	250	volts
Grid-No.2 Voltage	250	volts
Grid-No.1 (Control-Grid) Voltage ...	-12.5	volts
Peak AF Grid-No.1 Voltage	12.5	volts
Zero-Signal Plate Current	45	mA
Maximum-Signal Plate Current	47	mA
Zero-Signal Grid-No.2 Current	4.5	mA
Maximum-Signal Grid-No.2 Current ..	7	mA
Plate Resistance (Approx.)	50000	ohms
Transconductance	4100	μ mhos
Load Resistance	5000	ohms
Total Harmonic Distortion	8	per cent
Maximum-Signal Power Output	4.5	watts

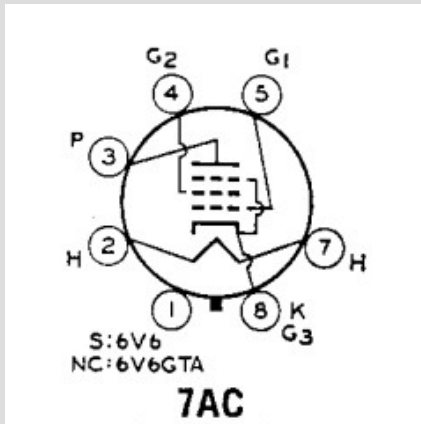

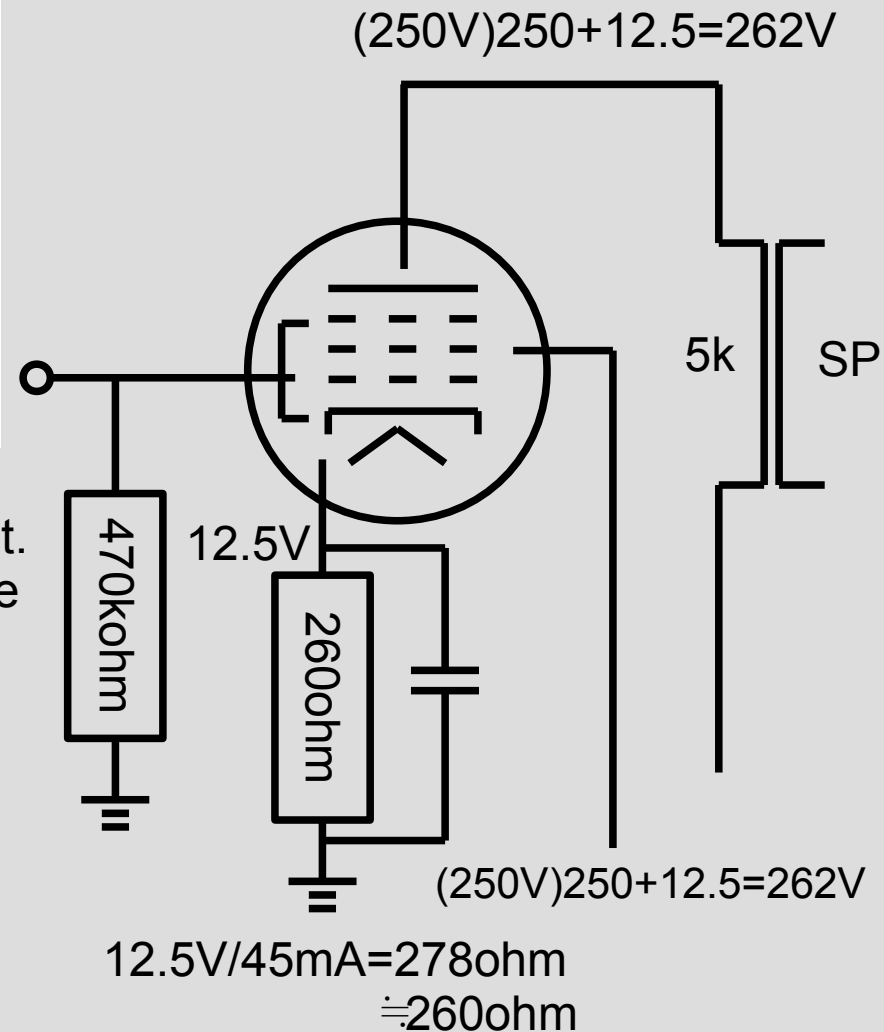
Depend on driver circuit.
Usually x2 the load of the
previous stage. Max
about 500k




Design for self bias 自己バイアス回路の設計

TYPICAL OPERATION

Plate Voltage	250	volts
Grid-No.2 Voltage	250	volts
Grid-No.1 (Control-Grid) Voltage	-12.5	volts
Peak AF Grid-No.1 Voltage	12.5	volts
Zero-Signal Plate Current	45	mA
Maximum-Signal Plate Current	47	mA
Zero-Signal Grid-No.2 Current	4.5	mA
Maximum-Signal Grid-No.2 Current	7	mA
Plate Resistance (Approx.)	50000	ohms
Transconductance	4100	μ mhos
Load Resistance	5000	ohms
Total Harmonic Distortion	8	per cent
Maximum-Signal Power Output	4.5	watts

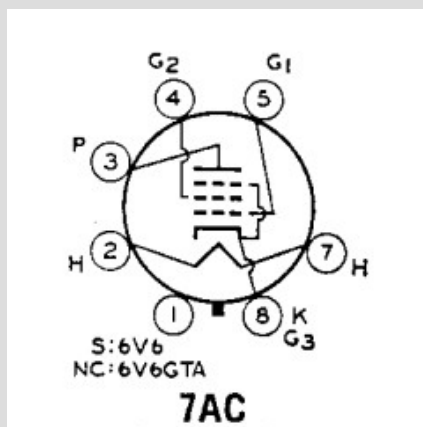

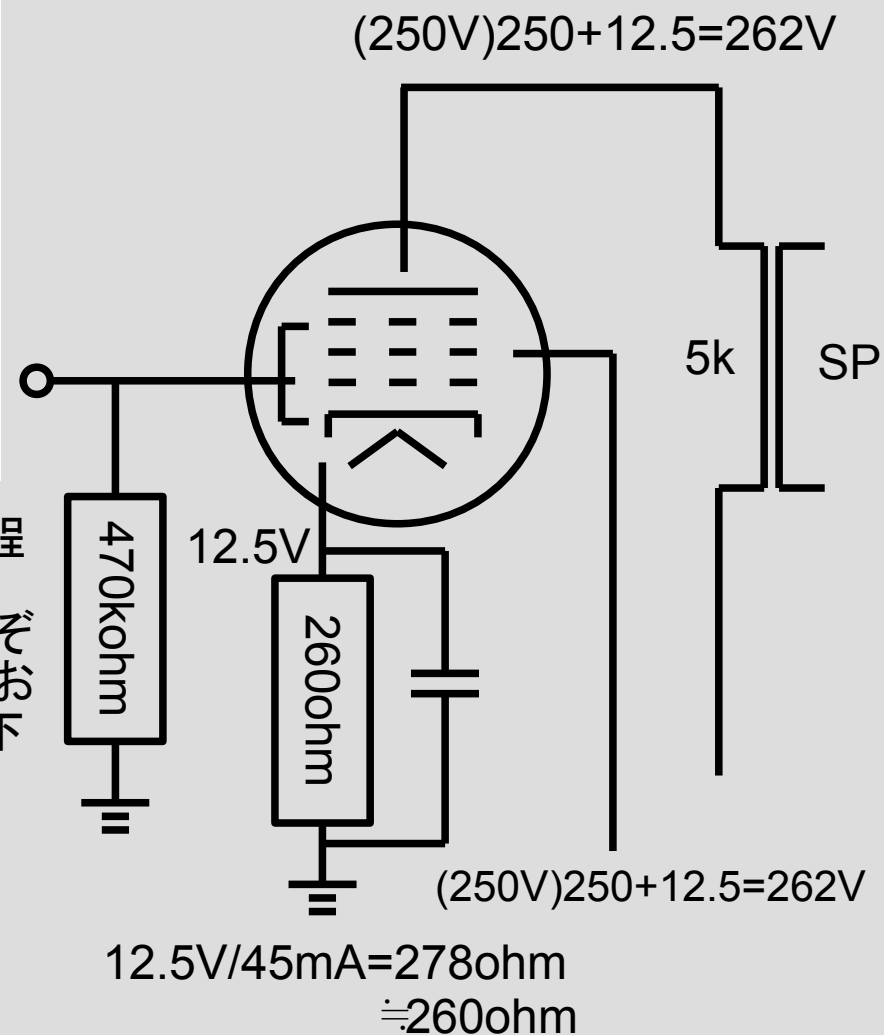
前段のプレート抵抗の倍程度の抵抗値を選びます。グリッドリーク抵抗はそれぞれの真空管で決められており6V6では最大500k Ω 以下と指示されている。




Design for fixed bias

TYPICAL OPERATION

Plate Voltage	250	volts
Grid-No.2 Voltage	250	volts
Grid-No.1 (Control-Grid) Voltage ...	-12.5	volts
Peak AF Grid-No.1 Voltage	12.5	volts
Zero-Signal Plate Current	45	mA
Maximum-Signal Plate Current	47	mA
Zero-Signal Grid-No.2 Current	4.5	mA
Maximum-Signal Grid-No.2 Current ..	7	mA
Plate Resistance (Approx.)	50000	ohms
Transconductance	4100	μ mhos
Load Resistance	5000	ohms
Total Harmonic Distortion	8	per cent
Maximum-Signal Power Output	4.5	watts

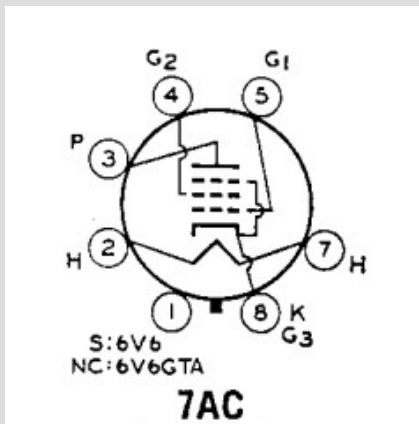

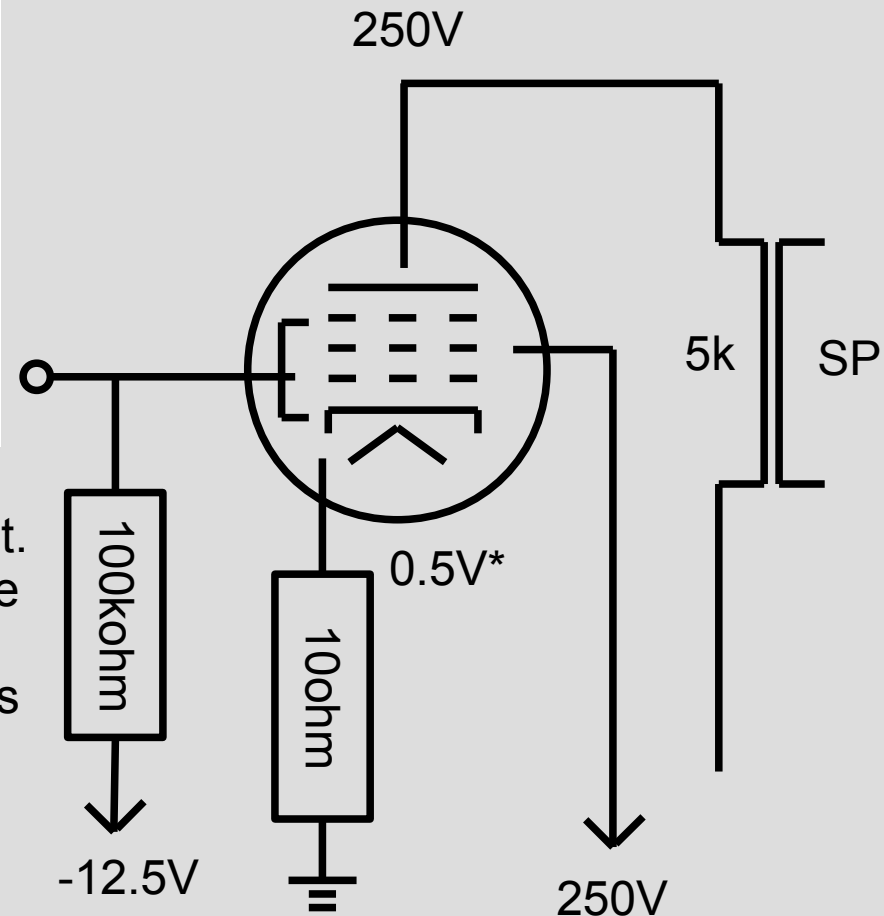Depend on driver circuit.
Usually x2 the load of the
previous stage. Max
about 100k for Fixed bias




$$0.5V^* = (45mA + 4.5mA) \times 10\text{ohm}$$


Design for fixed bias 固定バイアス回路の設計

TYPICAL OPERATION

Plate Voltage	250	volts
Grid-No.2 Voltage	250	volts
Grid-No.1 (Control-Grid) Voltage	-12.5	volts
Peak AF Grid-No.1 Voltage	12.5	volts
Zero-Signal Plate Current	45	mA
Maximum-Signal Plate Current	47	mA
Zero-Signal Grid-No.2 Current	4.5	mA
Maximum-Signal Grid-No.2 Current	7	mA
Plate Resistance (Approx.)	50000	ohms
Transconductance	4100	μmhos
Load Resistance	5000	ohms
Total Harmonic Distortion	8	per cent
Maximum-Signal Power Output	4.5	watts

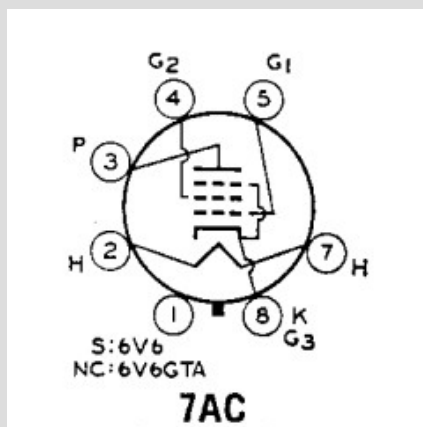

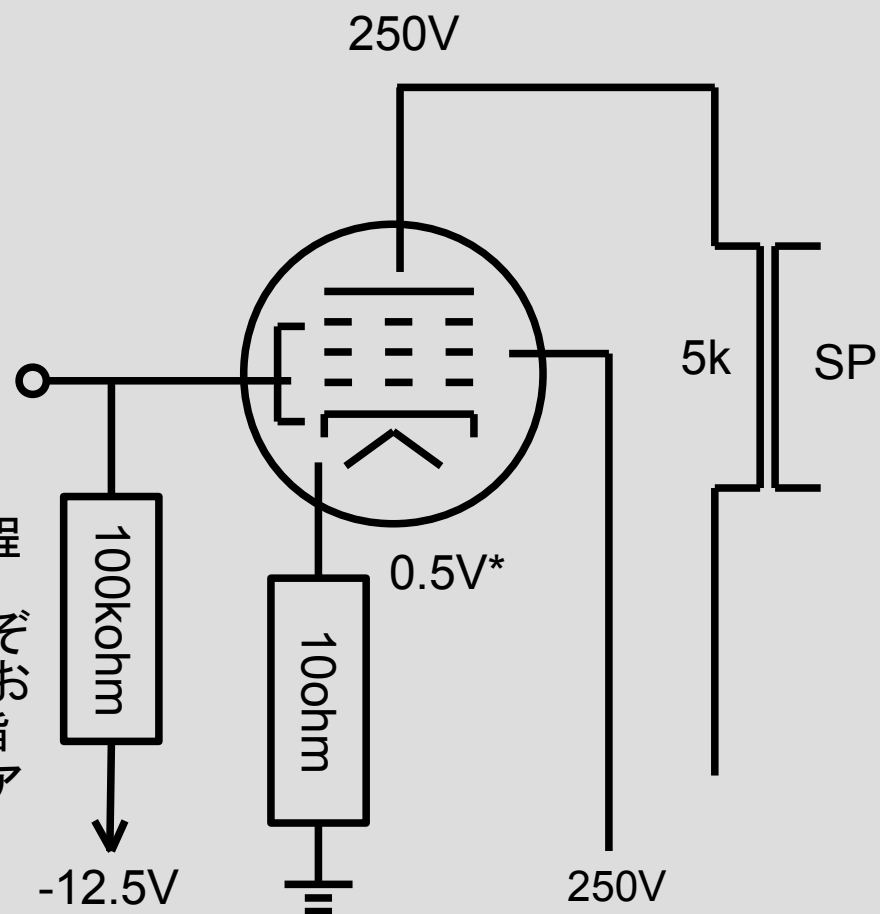前段のプレート抵抗の倍程度の抵抗値を選びます。グリッドリーク抵抗はそれぞれの真空管で決められており6V6では最大100k Ω と指示されている。(固定バイアス時)



$$0.5V^* = (45\text{mA} + 4.5\text{mA}) \times 10\text{ohm}$$

Recommend 5k single output trans from Japan

5kシングルトランスの紹介

- ISO
FC-12S(5k,12W)
FC-20S(5k,20W)
- General Trans
ゼネラルトランス
PMF-10WS(5k,10W)
PMF-20WS(5k,20W)
- Tamura
F912(5k,12W)



Thank you show my video
I am very happy. Your it. Channel registration.

ご覧いただきありがとうございます。

感想やご質問はコメント欄まで、また評価と
チャンネル登録お願いします。